

## **Video-1**

### **Objective:**

Measure various electrical properties such as voltage, current, and resistance within circuits using a single handheld instrument.

### **Uses:**

- Verifying battery voltage
- Measuring resistance of electronic components

### **Functions:**

- **DC Voltage:** Measures voltage from direct current sources
- **AC Voltage:** Measures voltage from alternating current sources
- **Current:** Measures the flow of current; requires connection in series
- **Resistance:** Determines resistance in components like resistors and wires

### **Types of Multimeters:**

- **Analog Multimeter:** Features a needle gauge; less commonly used today
  - **Digital Multimeter (DMM):** Displays readings on an LCD; more accurate and widely used
- 

## **Video-2:**

### **Objective:**

Regulate LED brightness through Pulse Width Modulation (PWM), demonstrated using a green LED.

### **Setup:**

- Green LED utilized
- Brightness controlled via PWM signal
- Duty cycle adjusted to vary intensity

### **Why PWM Dimming:**

- Offers efficient control of brightness
  - Preserves the LED's color quality
  - Produces less heat compared to resistive dimming
-

### **Video-3:**

#### **Objective:**

Program an ATtiny microcontroller using an Arduino as an ISP programmer with a custom-built shield.

#### **Components Used:**

- ATtiny85 microcontroller
- Arduino Uno (functioning as programmer)
- Homemade shield (ZIF socket or direct pin connection)
- 10 $\mu$ F capacitor between RESET and GND on Arduino

#### **Process:**

- Install ATtiny board support
  - Select ATtiny85 with 8 MHz clock
  - Upload “ArduinoISP” sketch to Uno
  - Insert ATtiny into custom shield
  - Use “Burn Bootloader” once
  - Upload code using “Upload Using Programmer” option
- 

### **Video-4:**

#### **Objective:**

Use text commands sent from an Android phone via Bluetooth to control LED colors.

#### **Components Used:**

- Arduino Uno
- Android phone (with Bluetooth terminal application)
- RGB LED or separate colored LEDs
- Resistors

#### **Working Principle:**

- User types a color name (e.g., “blue”) into the phone app
- Text is transmitted to Arduino via Bluetooth
- Arduino interprets the command and activates the corresponding LED

#### **Commands:**

- "blue" → Activates blue LED

- "green" → Activates green LED
  - "off" → Turns off all LEDs
- 

#### **Video-5:**

##### **Objective:**

Control a large quantity of LEDs arranged in a matrix using minimal Arduino pins.

##### **Concept Used:**

- Multiplexing
- Shift Registers
- LED Drivers

##### **Working Principle:**

- LEDs are structured in rows and columns (or 3D layers like in a cube)
  - Arduino activates one row/layer at a time at high speed
  - Shared connections reduce the number of pins required
  - Example: 8×8 matrix = 64 LEDs
  - Using shift registers, all LEDs can be controlled with just 3 Arduino pins
- 

#### **Video-6:**

##### **Objective:**

Operate Arduino-based projects without the full Arduino board—using only the microcontroller and essential components.

##### **Components:**

- ATmega microcontroller (from Arduino Uno)
- Power supply (battery or regulated 5V)
- 16 MHz crystal oscillator
- 22 picofarad capacitors
- 1k ohm resistor

##### **Working Principle:**

- After uploading the program to the ATmega chip, remove it from the Arduino board

- Place the chip onto a breadboard
  - It runs independently, saving both space and cost
- 

### **Video-7:**

#### **Objective:**

Display numerical values using 7-segment displays with the aid of driver ICs.

#### **Types of 7-Segment Displays:**

- **Common Cathode (CC):** All cathodes (grounds) connected together
- **Common Anode (CA):** All anodes (Vcc) connected together

#### **BCD to 7-Segment Driver:**

- Converts 4-bit Binary Coded Decimal (BCD) input into segment control signals
- Automatically illuminates segments to display digits 0–9
- Specifically designed for common cathode displays
- Minimizes Arduino pin usage (only 4 input pins required)

#### **SAA1064:**

- Utilizes I2C protocol for communication (only 2 wires: SDA and SCL)
  - Supports common cathode displays
  - Offers adjustable brightness settings
  - Ideal for compact, multi-digit numeric displays
- 

### **Video-8:**

#### **Objective:**

Ensure safe LED usage by calculating and applying current-limiting resistors.

#### **Why Resistors are Needed:**

- LEDs possess minimal internal resistance
- Without a resistor, excessive current may damage or destroy the LED
- Resistors regulate current flow to safe levels

#### **Kirchhoff's Laws:**

- **Kirchhoff's Current Law (KCL):** The sum of currents entering a junction equals the sum of currents leaving it—reflecting charge conservation

- **Kirchhoff's Voltage Law (KVL):** The total of voltage drops around any closed circuit loop equals zero—indicating energy conservation
- 

#### **Video-9:**

##### **Objective:**

Explore the operation of general-purpose diodes and their applications in both DC and AC circuits, especially power supplies.

##### **Key Facts:**

- Diodes allow current flow in one direction only (when forward-biased)
- Block current in the reverse direction (when reverse-biased)

##### **In AC Circuits:**

- Used for rectification—converting AC to DC
  - Single diode = half-wave rectifier
- 

#### **Video-10:**

##### **Objective:**

Convert binary digital signals into analog voltage outputs.

##### **8-bit R-2R Ladder DAC:**

- A straightforward and commonly used DAC circuit
- Constructed with just two resistor values: R and 2R
- Each of the 8 binary inputs contributes proportionally to the output voltage

##### **Voltage Follower (Op-Amp Buffer):**

- R-2R DAC outputs have high impedance
- Adding an op-amp in unity gain mode provides:
  - o Low output impedance
  - o Consistent voltage levels
  - o Isolation from loading effects

#### **Video-11:**

**Objective:**

Send SMS messages from an Arduino using the TC35 GSM module.

**TC35 GSM Module**

- A GSM communication module developed by Siemens
- Supports SMS, voice, and GPRS on 2G networks
- Communicates via serial interface (TX/RX)

**Operating Voltage:**

- Requires an external regulated 5V power supply
- Needs at least 2A current during transmission

**Connections**

- TC35 TX to Arduino RX is safe (uses 3.3V logic)
- 

**Video-12:****Objective:**

Understand how inductors (coils) behave in DC circuits and why they are vital in many electronic applications.

**Magnetic Field (MF):**

- When current flows through a coil, a magnetic field is created
- The field stores energy and resists sudden changes in current

**Electromagnetic Induction:**

- A changing magnetic field induces voltage in the coil or nearby coils
- This is the fundamental principle of energy conversion in inductors

**Inductance (L):**

- Measured in Henrys (H)
  - Indicates how strongly an inductor resists current changes
  - Inductors resist changes in current, not voltage
  - Always consider inductance, core material, and current rating
  - Used for energy storage, signal filtering, or component protection
-

### **Video-13:**

#### **Objective:**

Understand the concept of reactance in AC circuits, especially for inductors, and its impact on power and phase.

#### **Reactance:**

Reactance is the opposition inductors (or capacitors) provide to AC current.

**Unit:** Ohms ( $\Omega$ )

#### **Inductive Reactance Formula:**

$$X_L = 2\pi fL$$

Where:

- $f$  = frequency in Hz
- $L$  = inductance in Henrys (H)

#### **Reactive Power (Q):**

- Power temporarily stored and released by inductors or capacitors
- Measured in VARs (Volt-Ampere Reactive)

#### **Phase Shift (Inductive Circuits):**

- In inductors, current lags behind voltage
  - In pure inductance, voltage leads by  $90^\circ$
- 

### **Video-14:**

#### **Objective:**

Understand how capacitors function, what their ratings signify, and how they behave in different circuit types.

#### **How Capacitors Work:**

A capacitor stores electric energy as an electric field between two conductive plates separated by an insulator (dielectric).

#### **Electrolytic Capacitor Ratings:**

##### **1. Capacitance Value ( $\mu F$ ):**

- o Indicates the amount of charge the capacitor can store

## 2. **Voltage Rating (V):**

- o Maximum voltage the capacitor can withstand

## 3. **Polarity Marking:**

- o Electrolytic capacitors are polarized and must be correctly connected
- o A stripe indicates the negative pin (–)

### **Behavior in AC Circuits:**

- Current flows as voltage alternates direction
- Capacitor allows AC signals to pass, especially at higher frequencies

### **Capacitive Reactance (XC):**

- Opposition to AC current, based on frequency:

$$X_C = 1 / (2\pi fC)$$

- o Higher frequency = lower reactance
  - o Larger capacitance = less opposition
- 

### **Video-15:**

#### **Objective:**

Explore how material resistance changes with temperature.

#### **Resistance:**

- Many materials experience resistance variation with temperature
- This property can be measured and translated into a temperature reading
- Used in industrial, medical, and DIY electronics

### 1. **NTC Thermistors (Negative Temperature Coefficient):**

- Resistance drops as temperature rises
- Common, affordable, ideal for 0–100°C

### 2. **PT100 (Platinum Resistance Temperature Detector):**

- Platinum sensor with 100Ω at 0°C
- Resistance increases linearly with temperature
- Extremely accurate and reliable

### 3. **Wheatstone Bridge:**

- Detects small resistance changes
- Ideal for precise sensors like PT100



#### 4. **LM35 (Analog Temperature Sensor):**

- Outputs analog voltage at 10mV per °C
  - Easily read by Arduino's analog pins
- 

#### **Video-16:**

##### **Objective:**

Understand how resistors are practically used in electronic schematics for voltage, current control, and more.

##### 1. **Current Limiting Resistors**

Protect LEDs, transistors, and ICs by limiting current.

##### **Voltage Dividers**

Divide a voltage into smaller values.

- Useful for generating different voltage levels from one source
- Current remains the same through series components

##### 2. **Current Shunt Resistors**

Measure current by monitoring voltage drop.

**Ohm's Law:**  $V = IR$

##### 3. **Pull-Up and Pull-Down Resistors**

Set default HIGH or LOW logic levels on digital inputs.

##### 4. **Biasing Resistors**

Establish operating points for transistors in amplifier configurations.

---

#### **Video-17:**

##### **Objective:**

Understand why oscillators are essential and how three common types produce periodic signals.

##### 1. **RC Relaxation Oscillators**

Use a resistor-capacitor (RC) network to charge and discharge a capacitor, generating a repeating signal.

- Capacitor charges slowly through a resistor

## 2. **LC Tank Oscillators**

Use an inductor (L) and capacitor (C) to create a resonant circuit.

## 3. **Crystal Oscillators**

Use the mechanical resonance of a quartz crystal to produce a stable frequency.

---

### **Video-18:**

#### **Objective:**

Understand how a brushless motor spins using an Electronic Speed Controller (ESC).

#### 1. **DC Motor:**

- Stator: Permanent magnet
- Rotor (armature): Coils with brushes
- Brushes and commutator switch current mechanically

#### 2. **Brushless Motor (BLDC):**

- Stator: Stationary coils
- Rotor: Rotating permanent magnets

#### 3. **ESC (Electronic Speed Controller):**

- Controls speed using PWM (Pulse Width Modulation)
  - Sends precisely timed current pulses to the motor coils
- 

### **Video-19:**

#### **Objective:**

Learn how I2C (Inter-Integrated Circuit) allows communication between multiple devices using only two wires with Arduino.

#### 1. **I2C Overview:**

- Master (typically Arduino) manages communication
- Each slave device has a unique 7-bit address

#### 2. **Advantages of I2C:**

- Minimal pin usage

- Simplifies connection of multiple devices
  - Ideal for sensors, displays, and RTC modules
- 

## **Video-20:**

### **Objective:**

Understand what a thyristor is and how a TRIAC controls AC voltage in practical circuits.

#### **1. Thyristor:**

A diode that can be controlled

- Has three terminals: Anode, Cathode, and Gate

#### **2. TRIAC:**

A bidirectional thyristor

- Controls both positive and negative halves of an AC waveform
- Commonly used in AC dimming, motor speed regulation, or heating control

#### **3. TRIAC AC Control Circuit:**

##### **Components:**

- TRIAC
- Resistors and capacitor
- Load (e.g., lamp or fan)
- AC power source

## **Video-21**

### **Objective:**

Understand how OpAmps function and apply three key rules for circuit design.

### **Working:**

An OpAmp amplifies the voltage difference between its two inputs:

$$V_{out} = A(V_{+} - V_{-})$$

### **Rules:**

1. **No Input Current:**
    - $I_+ = I_- = 0$
  2. **Equal Input Voltage (with feedback):**
    - $V_+ = V_-$
  3. **High Gain ( $A \rightarrow \infty$ ):**
    - Ensures Rule 2 is upheld in feedback systems
- 

## Video-22

### Objective:

Use NPN and PNP transistors as electronic switches to control high-current loads with low-power signals.

### NPN as Low-Side Switch:

- Load connected between  $V_{cc}$  and Collector
- Base HIGH  $\rightarrow$  transistor conducts, load turns ON
- Base LOW  $\rightarrow$  transistor OFF

### PNP as High-Side Switch:

- Load connected between Emitter and  $V_{cc}$
  - Base HIGH  $\rightarrow$  transistor OFF
- 

## Video-23

### Objective:

Use MOSFETs as efficient electronic switches for controlling high-current loads using low-power control signals.

### N-Channel MOSFET – Low-Side Switch:

- Load connected between  $V_{cc}$  and Drain
- Source to GND
- Gate LOW  $\rightarrow$  Turns OFF

### P-Channel MOSFET – High-Side Switch:

- Load between Source and GND

- Source connected to Vcc
  - Gate close to Vcc → Turns OFF
- 

## **Video-24**

### **Objective:**

Understand how hybrid stepper motors work and how to control them with or without a microcontroller ( $\mu\text{C}$ ).

### **How It Works:**

- Hybrid stepper = combination of variable reluctance and permanent magnet motors
- Rotor has teeth and a permanent magnet → aligns precisely with stator's magnetic field
- Moves in fixed steps (e.g.,  $1.8^\circ$  per step)

### **How to Control:**

#### **Without Microcontroller:**

- Use stepper motor drivers (e.g., ULN2003, A4988)
- Provide step pulses manually using a 555 timer, switches, or logic gates

#### **With Microcontroller (Arduino, etc.):**

- Use driver modules
- 

## **Video-25**

### **Objective:**

Use a standard servo motor for precise angle control in projects, with or without a microcontroller.

### **How It Works:**

- Contains a DC motor, gears, potentiometer, and control circuit
- Controlled using PWM:
  - o  $1\text{ ms} = 0^\circ$ ,  $2\text{ ms} = 180^\circ$
  - o Signal repeated every 20 ms

### **Control Methods:**

**Without  $\mu\text{C}$ :**

- Use a 555 timer to generate PWM
  - Vary pulse width to control angle
- 

**Video-26****Objective:**

Understand how the 555 Timer IC works and how to use it in monostable, bistable, and astable modes for delay, toggle, or PWM generation.

**How It Works:**

- Contains a flip-flop, discharge transistor, and voltage divider
- Key pins:
  - o Trigger (2), Threshold (6), Discharge (7), Output (3)

**Monostable Mode:**

- Trigger pulse  $\rightarrow$  555 outputs HIGH for a fixed time

**Flip-Flop:**

- One input sets, another resets
- Used for switching or memory applications

**Oscillator:**

- In free-running mode  $\rightarrow$  generates a square wave
- 

**Video-27****Objective:**

Understand ADC (Analog-to-Digital Converter) specifications and how Successive Approximation Register (SAR) ADCs work.

**Specifications:**

- **Resolution (bits):** Number of discrete output levels
- **Sampling Rate:** Speed at which analog values are converted
- **Accuracy:** How closely output matches actual value

**SAR ADC Process:**

1. Sample analog input
  2. Comparator checks against internal DAC
  3. SAR logic adjusts each bit to refine the value
- 

## **Video-28**

### **Objective:**

Use an IGBT (Insulated Gate Bipolar Transistor) to switch loads, and understand when it outperforms MOSFETs.

- IGBT = MOSFET gate + BJT output stage
- Gate is controlled like a MOSFET (voltage-driven)

### **How to Use:**

- Gate drive method is similar to a MOSFET
  - Add gate resistor and possibly a gate driver IC
- 

## **Video-29**

### **Objective:**

Wire solar panels, use diodes for protection, and optimize charging using MPPT or PWM charge controllers.

### **Solar Panel Connections:**

- **Series:** Increases voltage
- **Parallel:** Increases current

### **Bypass Diodes:**

- Protect against shading → prevent power loss and hot spots
- Allow current to bypass shaded cells

### **Blocking Diodes:**

- Prevent reverse current flow from battery to panel at night

### **Maximizing Power Output:**

- Keep panels clean, angled properly, and unshaded

- Use MPPT (Maximum Power Point Tracking):
  - o Dynamically adjusts voltage for max power

#### **PWM Controller:**

- Connects panel directly to battery
- Simple and cost-effective, but less efficient

#### **MPPT Controller:**

- Converts excess voltage into additional current
  - Can be up to 30% more efficient in real-world use
- 

### **Video-30**

#### **Objective:**

Perform precise timing tasks and generate PWM signals using microcontroller timers.

#### **1. Timer1 or Timer2:**

- ATmega microcontrollers include Timer0, Timer1, and Timer2
- Timer1 is 16-bit

#### **At 8 MHz PWM:**

- If TOP = 1 → only 2 clock cycles per PWM cycle
- Duty cycle options are limited (0%, 50%, 100%)

#### **For higher resolution:**

- Reduce PWM frequency
- Or use an external timer/FPGA